

1. Use Newton-Raphson to find one solution to the polynomial equation $f(x) = x^3 - 9x^2 - 14x - 30 = 0$. Start with an initial guess of 0 and continue until the mismatch is below a tolerance of $\epsilon = 0.001$.

NR update method:

$$x^{(new)} = x^{(old)} - \frac{f(x^{(old)})}{f'(x^{(old)})}$$

$$f(x) = x^3 - 9x^2 - 14x - 30$$

$$f'(x) = 3x^2 - 18x - 14$$

$$x^{ini} = 0, \epsilon = 0.001 \text{ (Mismatch)}$$

First iteration:

$$x^{(0)} = x^{ini} = 0$$

$$f(x^{(0)}) = -30$$

$$f'(x^{(0)}) = -14$$

$$x^{(1)} = x^{(0)} - \frac{f(x^{(0)})}{f'(x^{(0)})} = 0 - \left(\frac{-30}{-14} \right) = -2.143$$

$$\text{Check: } f(x^{(1)}) = (-2.143)^3 - 9(-2.143)^2 - 14(-2.143) - 30 = -51.17$$

$$|f(x^{(1)})| = 51.17 > \epsilon, \text{ hence do second iteration}$$

Second iteration

$$x^{(2)} = x^{(1)} - \frac{f(x^{(1)})}{f'(x^{(1)})}$$

$$f(x^{(1)}) = -51.17$$

$$f'(x^{(1)}) = +38.35$$

$$x^{(2)} = -2.143 - \left(\frac{-51.17}{+38.35} \right) = -2.143 + 1.334 = -0.809$$

$$\text{Check: } f(x^{(2)}) = (-0.809)^3 - 9(-0.809)^2 - 14(-0.809) - 30 = -25.09$$

$$|f(x^{(2)})| = 25.09 > \epsilon, \text{ hence do third iteration}$$

Continue iteration until $|f(x)| < \epsilon$

After 7 iterations,

$$x^{(7)} = 10.59$$

$$\text{and } |f(x^{(7)})| = 2.97 \times 10^{-6} < \epsilon$$

2. The following nonlinear equations contain terms that are often found in the power flow equations:

$$f_1(\mathbf{x}) = 12 x_1 \sin x_2 + 1.5 = 0$$

$$f_2(\mathbf{x}) = 12 (x_1)^2 - 12 x_1 \cos x_2 + 0.75 = 0$$

Start with an initial guess of $x_1(0) = 1$ and $x_2(0) = 0$ radians, and a stopping criteria of $\epsilon = 10^{-4}$.

$$\bar{\mathbf{x}}^{ini} = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}^{(0)} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad \epsilon (\text{Mismatch}) = 10^{-4}$$

NR update

$$\begin{bmatrix} x_1 \\ x_2 \end{bmatrix}^{(new)} = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}^{old} - \begin{bmatrix} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} \end{bmatrix}^{-1} \begin{bmatrix} f_1(\bar{\mathbf{x}}^{old}) \\ f_2(\bar{\mathbf{x}}^{old}) \end{bmatrix}; \quad \bar{\mathbf{x}} = [x_1, x_2]$$

$$\frac{\partial f_1}{\partial x_1} = 12 \sin x_2; \quad \frac{\partial f_1}{\partial x_2} = 12 x_1 \cos x_2$$

$$\frac{\partial f_2}{\partial x_1} = 24 x_1 - 12 \cos x_2; \quad \frac{\partial f_2}{\partial x_2} = 12 x_1 \sin x_2$$

First iteration:

Compute entries for Jacobian, $[J(x)]$ and mismatch

$$\frac{\partial f_1}{\partial x_1}^{old} = 0; \quad \frac{\partial f_1}{\partial x_2}^{old} = 12$$

$$\frac{\partial f_2}{\partial x_1}^{old} = 12; \quad \frac{\partial f_2}{\partial x_2}^{old} = 0$$

$$f_1(\bar{\mathbf{x}}^{old}) = 1.5, \quad f_2(\bar{\mathbf{x}}^{old}) = 0.75$$

$$\text{Hence, } \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}^{(1)} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} - \begin{bmatrix} 0 & 12 \\ 12 & 0 \end{bmatrix}^{-1} \begin{bmatrix} 1.5 \\ 0.75 \end{bmatrix} = \begin{bmatrix} 0.9375 \\ -0.125 \end{bmatrix}$$

$$\text{Check: } \begin{bmatrix} f_1(\bar{\mathbf{x}}^{(1)}) \\ f_2(\bar{\mathbf{x}}^{(1)}) \end{bmatrix} = \begin{bmatrix} 12(0.9375)\sin(-0.125) + 1.5 \\ 12(0.9375)^2 - 12(0.9375)\cos(-0.125) + 0.75 \end{bmatrix} = \begin{bmatrix} 0.097 \\ 0.135 \end{bmatrix}$$

$$f_1(\bar{x}^{(4)}) = 0.097 > 10^{-4}$$



and

$$f_2(\bar{x}^{(4)}) = 0.135 > 10^{-4}$$

Hence continue with second iteration

After 4 iterations, arrive at $\begin{bmatrix} x_1 \\ x_2 \end{bmatrix}^{(4)} = \begin{bmatrix} 0.923 \\ -0.136 \end{bmatrix}$, and $f_1(\bar{x}^{(4)}), f_2(\bar{x}^{(4)}) < 10^{-4}$

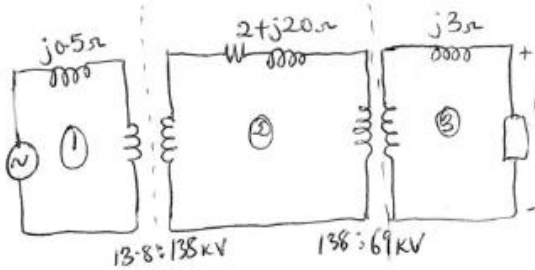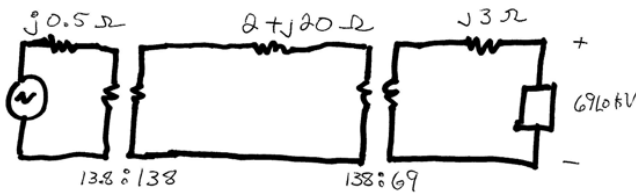3. Assume the below diagram models a balanced three-phase system in which a $120 + j60$ MVA load (total for all three phases) is supplied at 69 kV (line-to-line). First, redraw the network using a per unit representation with a 100 MVA base, and a 69 kV voltage base for the load. How much real and reactive power is being supplied by the generator (source) on the left?



$$S_L = 120 + j60 \text{ MVA}$$

$$S_B = 100 \text{ MVA}$$

$$Z_B = \frac{V_B^2}{S_B} \text{ (Here, } V_B \text{ is in kV)}$$

$$V_{B1} = V_{B2} \times \frac{13.8}{138}$$

$$= 13.8 \text{ kV}$$

$$Z_{B1} = \frac{V_{B1}^2}{S_B} = 1.9 \Omega$$



$$V_{B2} = V_{B3} \times \frac{138}{69} = 138 \text{ kV}$$

$$Z_{B2} = \frac{V_{B2}^2}{S_B} = 190.4 \Omega$$

$$V_{B3} = 69 \text{ kV}$$

$$Z_{B3} = \frac{V_{B3}^2}{S_B} = \frac{69^2}{100} = 47.6 \Omega$$

Per unit representation

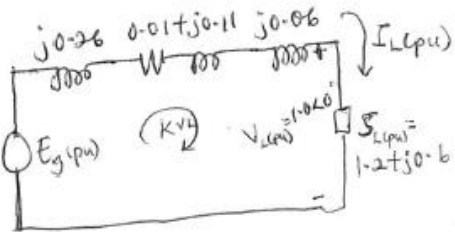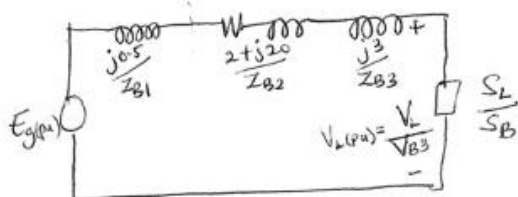

From load,

$$S_L(\text{pu}) = V_L(\text{pu}) \times I_L^*(\text{pu})$$

$$I_L(\text{pu}) = \left(\frac{S_L(\text{pu})}{V_L(\text{pu})} \right)^* = \left(\frac{1.2 + j0.6}{1.0 \angle 0^\circ} \right)^* = 1.2 - j0.6 \text{ pu}$$

Using KVL,

$$\begin{aligned} E_g(\text{pu}) &= V_L(\text{pu}) + I_L(\text{pu}) (j0.26 + j0.01 + j0.11 + j0.06) \\ &= 1.0 \angle 0^\circ + (1.2 - j0.6)(0.01 + j0.43) \\ &= 1.27 + j0.51 \end{aligned}$$

Power generated from source

$$\begin{aligned} S_g(\text{pu}) &= E_g(\text{pu}) I_L^*(\text{pu}) = (1.27 + j0.51)(1.2 - j0.6)^* \\ &= 1.218 + j1.374 \text{ pu} \end{aligned}$$


$$S_g(\text{pu}) = P_g(\text{pu}) + jQ_g(\text{pu}) \equiv 1.218 + j1.374 \text{ pu}$$

Hence, real $P_g(\text{pu}) = 1.218 \text{ pu}$ OR 121.8 MW

reactive $Q_g(\text{pu}) = 1.374 \text{ pu}$ OR 137.4 MVar

4. In the space on the next page determine the bus admittance matrix (Y_{bus}) for the following power system (note that some of the values have already been determined for you). Except where noted otherwise, assume all values are per unit using a 100 MVA base.

Sample System

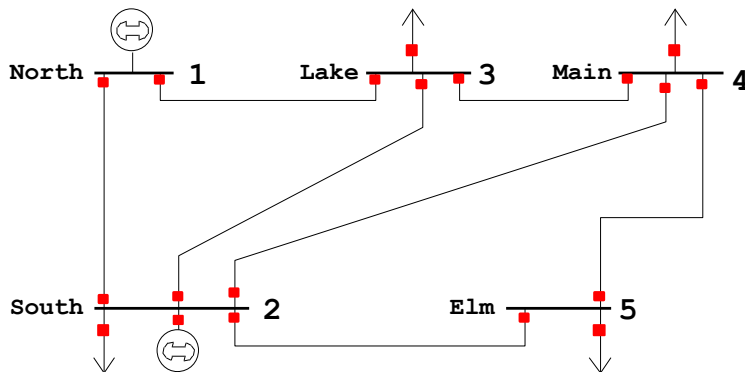

Line impedances and charging values

From/to buses	Impedance Z_{ij}	Line Charging $Y/2$
1-2	$0.02 + j 0.06$	$j 0.030$
1-3	$0.08 + j 0.24$	$j 0.025$
2-3	$0.06 + j 0.18$	$j 0.020$
2-4	$0.08 + j 0.24$	$j 0.025$
2-5	$0.02 + j 0.06$	$j 0.010$
3-4	$0.04 + j 0.12$	$j 0.015$
4-5	$0.06 + j 0.18$	$j 0.020$

$$\begin{aligned}
Y_{12} = Y_{21} &= -\frac{1}{Z_{12}} & Y_{11} &= \frac{1}{Z_{12}} + \frac{1}{Z_{13}} + j0.03 + j0.025 \\
Y_{13} = Y_{31} &= -\frac{1}{Z_{13}} & Y_{22} &= \frac{1}{Z_{12}} + \frac{1}{Z_{23}} + \frac{1}{Z_{24}} + \frac{1}{Z_{25}} + j0.03 + j0.02 + j0.025 + j0.01 \\
Y_{23} = Y_{32} &= -\frac{1}{Z_{23}} & Y_{33} &= \frac{1}{Z_{13}} + \frac{1}{Z_{34}} + j0.025 + j0.015 + \frac{1}{Z_{23}} + j0.02 \\
Y_{24} = Y_{42} &= -\frac{1}{Z_{24}} & Y_{44} &= \frac{1}{Z_{24}} + \frac{1}{Z_{34}} + \frac{1}{Z_{45}} + j0.025 + j0.015 + j0.02 \\
Y_{25} = Y_{52} &= -\frac{1}{Z_{25}} & Y_{55} &= \frac{1}{Z_{25}} + \frac{1}{Z_{45}} + j0.01 + j0.02 \\
Y_{34} = Y_{43} &= -\frac{1}{Z_{34}} & & \\
Y_{45} = Y_{54} &= -\frac{1}{Z_{45}} & & \\
Y_{11} &= \frac{1}{Z_{12}} + \frac{1}{Z_{13}} + j0.03 + j0.025 & &
\end{aligned}$$

Bus admittance matrix (Y_{bus})

6.25 - j 18.695	-5.00 + j 15.00	-1.25 + j 3.75	0	0
-5.00 + j 15.00	12.9167 - j38.6650	-1.6667 + j5.0000	-1.2500 + j3.7500	-5.0000 + j15.0000
-1.2500 + j3.7500	-1.6667 + j5.0000	5.4167 - j16.1900	-2.5000 + j7.5000	0
0	-1.2500 + j3.7500	-2.5000 + j7.5000	5.4167 - j16.1900	-1.6667 + j5.0000
0	-5.0000 + j15.0000	0	-1.6667 + j5.0000	6.6667 - j19.9700

Now assume that a 0.5 per unit shunt resistance is added at bus 3 (i.e., on each phase a 0.5 per unit resistance is connected phase to ground). Calculate the new value of y_{33} :

$$y_{33}(\text{new}) = y_{33}(\text{old}) + (1/0.5) = \mathbf{7.4167 - 16.1900i}$$

Do any other values of Y_{bus} change? **No**

Now assume that a 75 Mvar (three phase) shunt capacitance is added at bus 4. Calculate the new value of y_{44} :

Since no transformer is present on any side of the network, we can assume voltage at all buses (bus 4 inclusive) to be 1.0 p.u. Also, in per unit, $Q_c = j0.75$, and from $Q_c = V^2 * B$, $B = j0.75$

$$y_{44}(\text{new}) = y_{44}(\text{old}) + j0.75 = \mathbf{5.4167 - j15.44}$$

5. Using PowerWorld Simulator and the case ECEN_615_HW1, give the bus numbers and circuit of two transmission lines that when opened cause at least one other line to be overloaded.

Among different, possible transmission line outages are:

Example Case	Disconnected		Circuit	Overloaded line		Circuit	Percent
	From	To	Num	From	To	Num	Line Loading
1	Pecan69	Pear 69	1	Pecan69	Pear 69	3	148
	Pecan69	Pear 69	2				
2	Cedar69	Olive69	2	Cedar69	Olive69	1	135
	Redbud69	Cherry69	1				
3	Peach69	Poplar69	1	Oak69	Walnut69	1	106
4	Elm345	Slack345	1	Elm138	Lemon138	1	102
	Elm138	Peach138	1				
5	Birch69	Lemon69	1	Cedar69	Olive69	1	114
	Peach69	Redbud69	1	Cedar69	Olive69	2	114